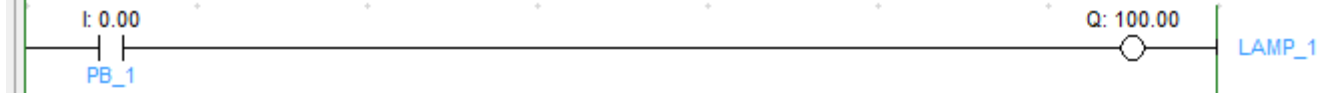


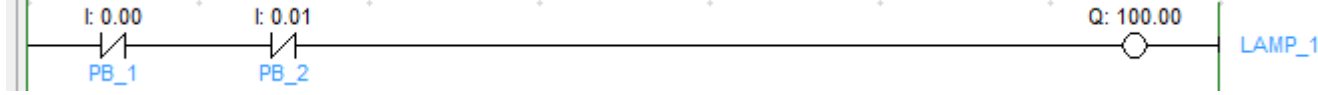
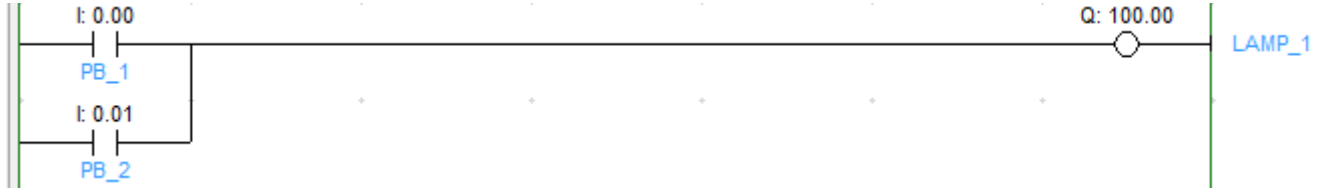

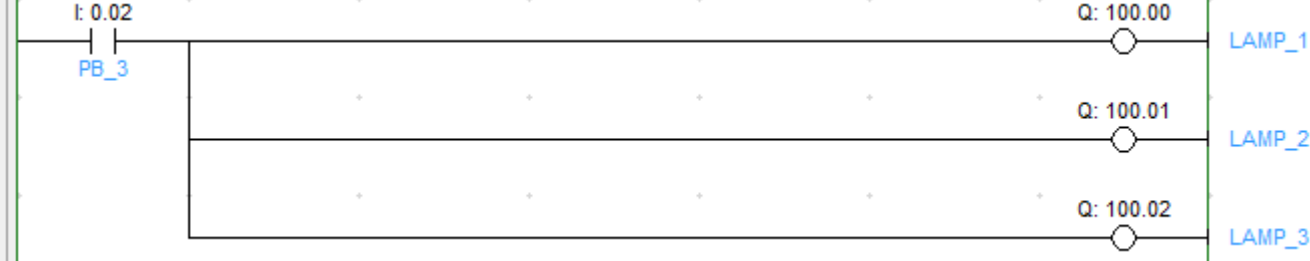




# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
1	LD INSTRUCTION 	LD 0.00 OUT 100.00
2	LDNOT INSTRUCTION 	LDNOT 0.00 OUT 100.00
3	AND INSTRUCTION 	LD 0.00 AND 0.01 OUT 100.00
4	ANDNOT INSTRUCTION 	LDNOT 0.00 ANDNOT 0.01 OUT 100.00
3	OR INSTRUCTION 	LD 0.00 OR 0.01 OUT 100.00

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
4	<p>ORNOT INSTRUCTION</p> 	LDNOT 0.00 ORNOT 0.01 OUT 100.00
5	<p>MULTIPLE OUTPUT</p> 	LD 0.02 OUT 100.00 OUT 100.01 OUT 100.02
6	<p>ANDLD</p> 	LD 0.00 OR 0.02 LD 0.01 OR 0.03 ANDLD OUT 100.03
7	<p>ORLD</p> 	LD 0.00 AND 0.01 LD 0.02 AND 0.03 ORLD OUT 100.04

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
8	<p>LATCHING (SELF HOLDING)</p>	LD 0.00 OR 100.02 ANDNOT 0.01 OUT 100.02
9	<p>INTERLOCK</p>	LD 0.00 OR 100.00 ANDNOT 0.02 ANDNOT 100.01 OUT 100.00 LD 0.01 OR 100.01 ANDNOT 0.02 ANDNOT 100.00 OUT 100.01
10	<p>WORK BIT (INTERNAL RELAY)</p>	LD 0.01 OR W10.00 ANDNOT 0.02 OUT W10.00 LD W10.00 OUT 100.00 LDNOT W10.00 OUT 100.01

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
11	<p>SET RSET INSTRUCTION</p>	LD 0.00 SET W10.01 LD 0.01 RSET W10.01 LD W10.01 OUT 100.03
12	<p>KEEP INSTRUCTION</p>	LD 0.01 LD 0.02 KEEP W10.02 LD W10.02 OUT 100.04

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
13	<p>DIFFERENTIATE UP (DIFU) INSTRUCTION</p>	<pre> LD 0.00 DIFU W10.00 LD W10.00 OR 100.01 ANDNOT 0.01 OUT 100.01 </pre>
14	<p>DIFFERENTIATE DOWN (DIFD) INSTRUCTION</p>	<pre> LD 0.00 DIFD W10.00 LD W10.00 OR 100.01 ANDNOT 0.01 OUT 100.01 </pre>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
15	<p><b>TIMER INSTRUCTION – DELAY TO ON</b></p>	<pre> LD 0.00 TIM 00     #50 LD T000 OUT 100.02         </pre>
16	<p><b>TIMER INSTRUCTION – DELAY TO OFF</b></p>	<pre> LD 0.01 OR W10.01 OUT TR0 ANDNOT T001 OUT W10.01 LD TR0 ANDNOT 0.01 TIM 001     #50 LD W10.01 OUT 100.02         </pre>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
17	<p>TIMER INSTRUCTION – ON/OFF DELAY</p>	<p>LD 0.00 TIM 000 #50 LD 100.03 ANDNOT 0.00 TIM 001 #70 LD T000 LD T001 KEEP 100.03</p>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC



NO	LADDER DIAGRAM	INSTRUCTION LIST
18	<p>TIMER INSTRUCTION – FLICKER</p>	<pre> LD 0.00 OR W10.00 ANDNOT 0.01 OUT W10.00 LD W10.00 ANDNOT TIM001 TIM 000     #10 LD T000 TIM 001     #10 LD T000 OUT 100.03 </pre>





# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
19	<p><b>TIMER INSTRUCTION – FLICKER</b></p>	<pre> LD 0.00 OR W10.00 OR T001 ANDNOT 0.01 ANDNOT T000 OUT W10.00 TIM 000 #10 LD T000 OR W10.01 ANDNOT 0.01 ANDNOT T001 OUT W10.01 TIM 001 #10 LD W10.00 OUT 100.04 </pre>
20	<p><b>TIMER INSTRUCTION – FLICKER (USING SPECIAL RELAY)</b></p>	<pre> LD 0.01 AND P_1s OUT 100.03 </pre>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

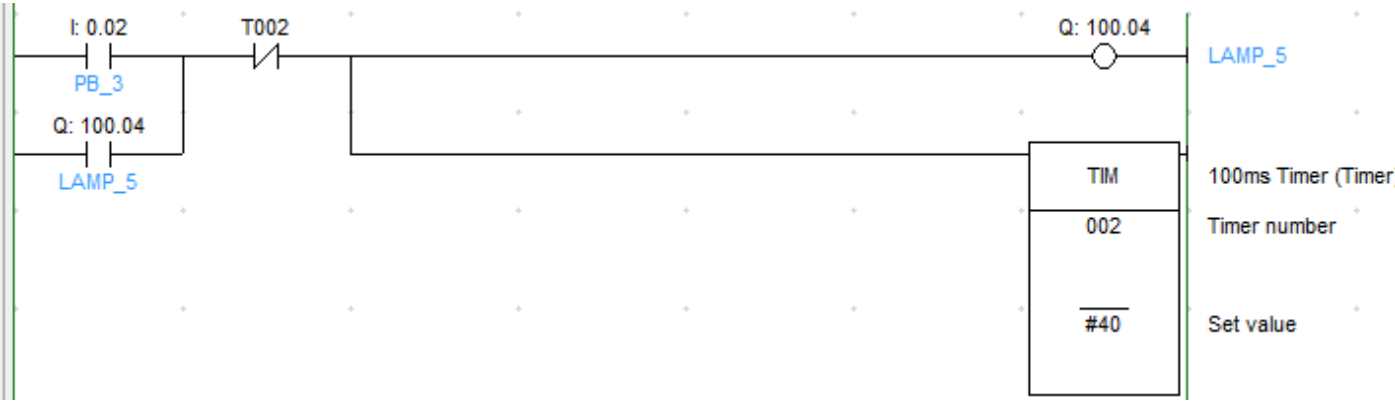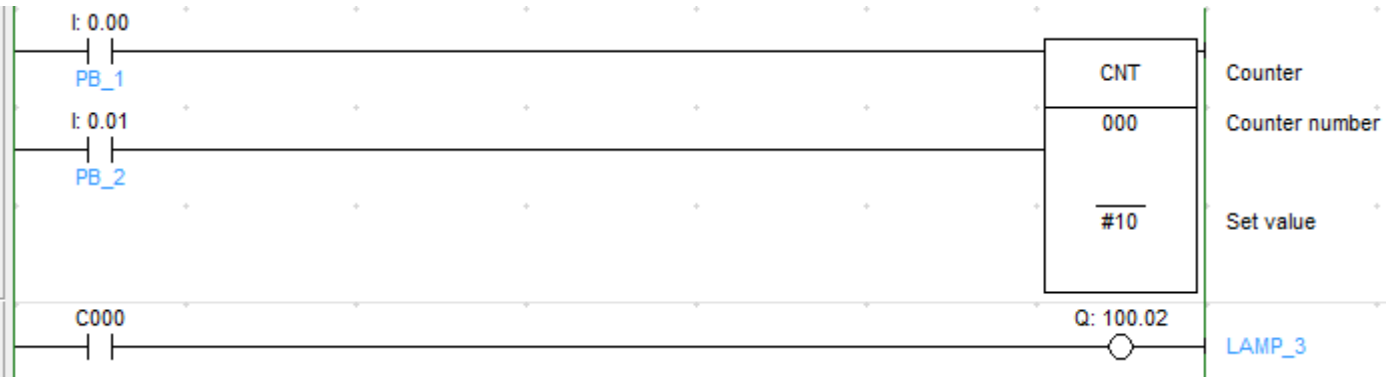NO	LADDER DIAGRAM	INSTRUCTION LIST
21	<p>TIMER INSTRUCTION – LATCHING (AUTO OFF)</p> 	<p>LD 0.02 OR 100.04 ANDNOT T002 OUT 10004 TIM 002 #40</p>
22	<p>COUNTER INSTRUCTION -1</p> 	<p>LD 0.00 LD 0.01 CNT 000 #10 LD C000 OUT 100.02</p>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

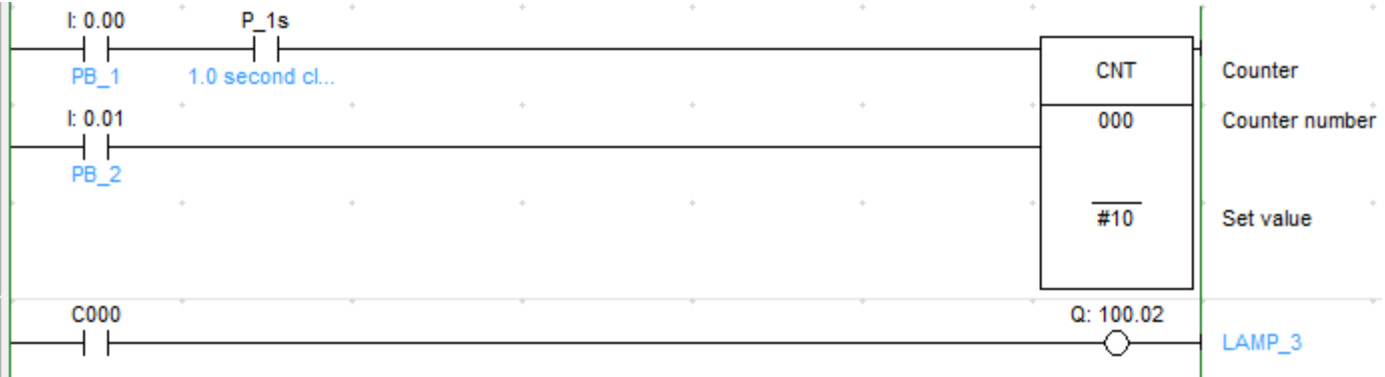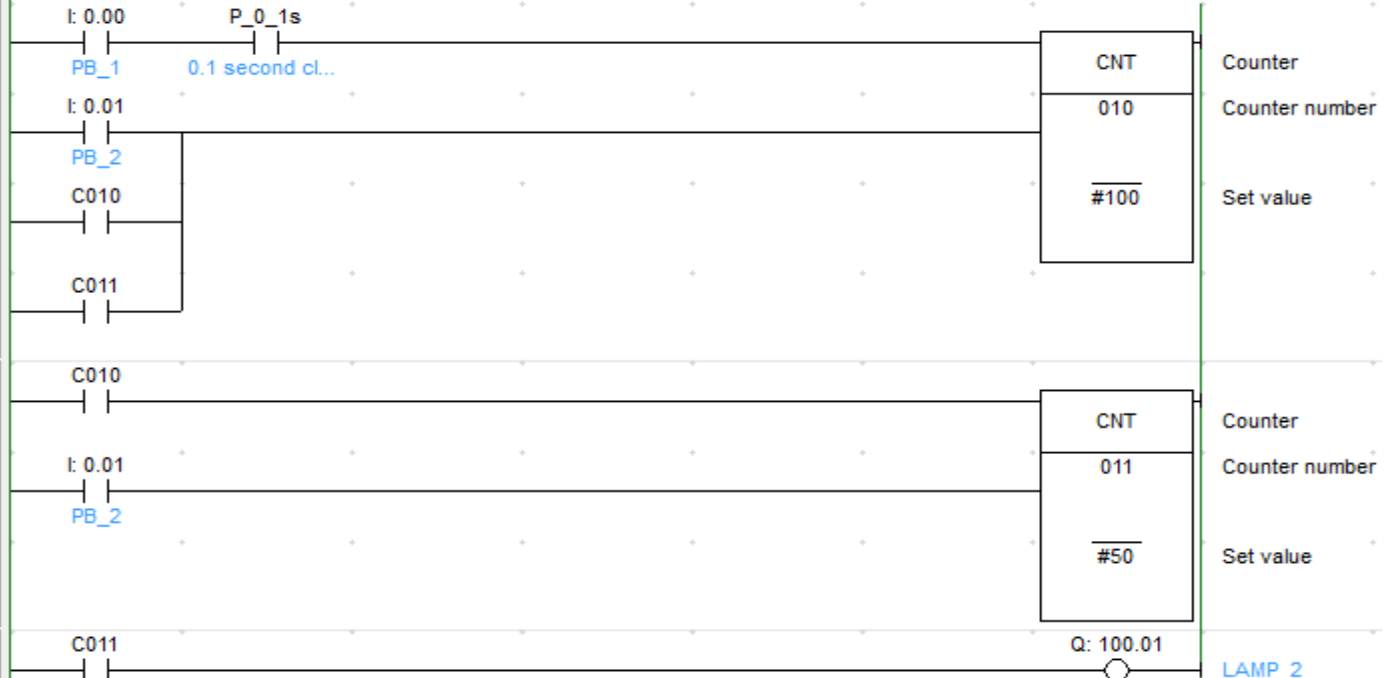NO	LADDER DIAGRAM	INSTRUCTION LIST
23	<p>COUNTER INSTRUCTION -2</p> 	<pre> LD 0.00 AND P_1s LD 0.01 CNT 000 #10 LD C000 OUT 100.02 </pre>
24	<p>COUNTER INSTRUCTION – EXTENDED COUNTER</p> 	<pre> LD 0.00 AND P_0_1s LD 0.01 OR C010 OR C011 CNT 010 #100 LD C010 LD 0.01 CNT 011 #50 LD C011 OUT 100.01 </pre>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
25	<p>COUNTER INSTRUCTION –EXTENDED TIMER USING COUNTER AND TIMER</p>	<pre> LD 0.00 ANDNOT T000 ANDNOT C001 TIM 000 #10 LD T000 LD 0.01 CNT 001 #10 LD C001 OUT 100.02 </pre>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
26	<p>EXTENDED TIMER USING TIMER INSTRUCTION IN SERIES CONNECTION</p> <p>The ladder diagram consists of four rungs. The first rung starts with a normally open contact labeled 'I: 0.00' and 'PB_1', followed by a timer coil labeled 'TIM 000' with a set value of '#100'. The second rung starts with a normally open contact labeled 'T000', followed by a timer coil labeled 'TIM 001' with a set value of '#50'. The third rung starts with a normally open contact labeled 'T001', followed by a timer coil labeled 'TIM 002' with a set value of '#20'. The fourth rung starts with a normally open contact labeled 'T002', followed by a coil labeled 'Q: 100.04' and 'LAMP_5'.</p>	<p>LD 0.00  TIM 000  #100  LD T000  TIM 001  #50  LD T001  TIM 002  #20  LD T002  OUT 100.04</p>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
27	<p>ON OFF SINGLE BUTTON USING COUNTER INSTRUCTION</p>	<p>LD 0.00  LD C001  CNT 000  #1  LD 0.00  LD C001  CNT 001  #2  LD C000  OUT 100.03</p>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
28	ON OFF SINGLE BUTTON – 1	<div> <pre> graph TD     subgraph Rung1 [Rung 1]         I000[I: 0.00] --- J1(( ))         W1000[W10.00] --- J1         J1 --- W1000_CO[W10.00]     end     subgraph Rung2 [Rung 2]         W1000_NO[W10.00] --- J2(( ))         I000_NC[I: 0.00] --- J2         J2 --- W1001_CO[W10.01]     end     subgraph Rung3 [Rung 3]         W1001_NO[W10.01] --- J3(( ))         I000_NC2[I: 0.00] --- J3         J3 --- W1002_CO[W10.02]     end     subgraph Rung4 [Rung 4]         W1002_NO[W10.02] --- J4(( ))         I000_NC3[I: 0.00] --- J4         J4 --- W1003_CO[W10.03]     end     subgraph Rung5 [Rung 5]         W1000_NO2[W10.00] --- Q10000[Q: 100.00]     end                     </pre> <p>1ST_PUSH</p> <p>SIGNAL FOR 2ND</p> <p>2ND_PUSH</p> <p>RESTART CYCLE</p> <p>LAMP_1</p> </div>

# LADDER DIAGRAM EXAMPLES USING CX-PROGRAMMER AND OMRON CP1E PLC

NO	LADDER DIAGRAM	INSTRUCTION LIST
28	ON OFF SINGLE BUTTON – 1	<pre> LD 0.00 OUT TR0 LDNOT 100.00 OR W0.01 ANDLD ANDNOT W0.02 OUT W0.01 LD TR0 LD 100.00 OR W0.02 ANDLD ANDNOT W0.01 OUT W0.02 LD 100.00 OR W0.01 ANDNOT W0.02 OUT 100.00 </pre>